

Student Name: EGE CAN KAYA

Student ID: 2018400018

Session: 2

CMPE 240 2020 Experiment 5 Preliminary Work

1. State Register Inputs: $n0 = xs0 + x's1$
 $n1 = xs0's1' + s0s1$
2. State Register Outputs: $s0$
 $s1$
3. Combinational Block Inputs: x
4. Combinational Block Output: $y0 = x's0's1' + xs0s1'$
 $y1 = x's1$
5. Fill the following truth table:

#	s1	s0	x	n1	n0	y1	y0
0	0	0	0	0	0	0	1
1	0	0	1	1	0	0	0
2	0	1	0	0	0	0	0
3	0	1	1	0	1	0	1
4	1	0	0	0	1	1	0
5	1	0	1	0	0	0	0
6	1	1	0	1	1	1	0
7	1	1	1	1	1	0	0

6. Is this a Moore or Mealy Machine? (No explanation, only short answer)


It is a Mealy machine.

Student Name: EGE CAN KAYA

Student ID: 2018400018

Session: 2

7. Draw the FSM:

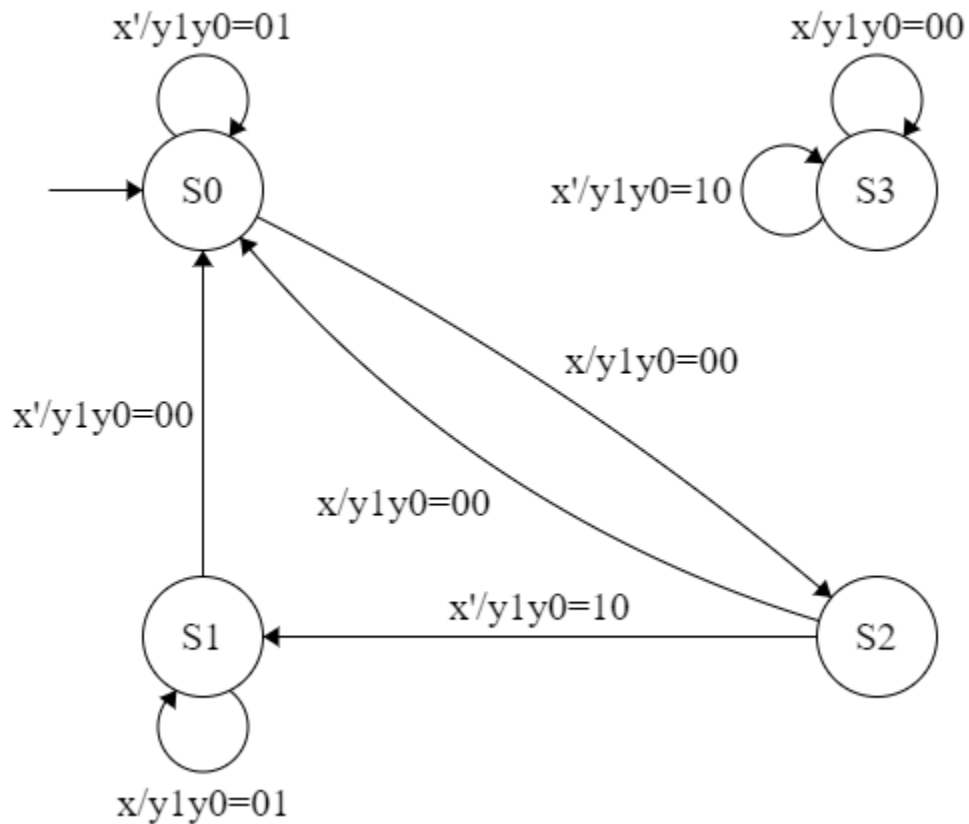

8. How many unreachable states does the finite state machine contain?

It contains 1 unreachable state: S3.

9. Minimize the state machine. Show your steps. Is it minimized or not?

S1			
S2			
S3			
	S0	S1	S2

Student Name: EGE CAN KAYA

Student ID: 2018400018

Session: 2

S1			
S2			
S3			x': (S3, S1) x: (S3, S0)
	S0	S1	S2

S1			
S2			
S3			x': (S3, S1) x: (S3, S0)
	S0	S1	S2

The FSM cannot be minimized any further. It is already minimal.